

III sem B.Tech(CCE)
2171 Digital systems and computer organisation

- **Topics covered**
- MINTERM, MAXTERM
- Writing Boolean expressions for the given truth table
- Design of a combinational circuit for the given problem

MINTERMS & MAXTERMS

- MIN and MAX are means to represent the inputs through logical AND /OR operations
- Consider a 3-variable Boolean function, $F(a,b,c)$
- Prepare a table with 6 columns
- In first column, write all possible binary combinations, possible with three input variables, one below the other. Ex:000,001....., .. . 111
- In 2nd column, write decimal equivalent of all the corresponding input combinations.

m_5 m_4 m_3 m_2 m_1 m_0
 2^2 2^1 2^0
 $=4$ $=2$ $=1$
 a b c

LSB

Rough

Least significant bit

		(MINTERM)		(MAXTERM)	
✓ 0 0 0	0	$(\bar{a}\bar{b}\bar{c}) \rightarrow m_0$		$(a+b+c)$	M_0
0 0 1 ✓	1	$\bar{a}\bar{b}c \rightarrow m_1$		$(a+b+\bar{c})$	M_1
0 1 0 ✓	2	$\bar{a}b\bar{c} \rightarrow m_2$		$(a+b+c) = 0$	
0 1 1	3	$\bar{a}bc \rightarrow m_3$		$(a+\bar{b}+c)$	m_2
1 0 0	4	$ab\bar{c} \rightarrow m_4$		$(\bar{a}+b+\bar{c})$	m_3
1 0 1	5	$abc \rightarrow m_5$		$(\bar{a}+b+c)$	m_4
1 1 0	6	$ab\bar{c} \rightarrow m_6$		$(\bar{a}+b+\bar{c})$	m_5
1 1 1	7	$abc \rightarrow m_7$		$(\bar{a}+\bar{b}+c)$	m_6
				$(\bar{a}+\bar{b}+\bar{c})$	m_7

Minterms (Standard products) and Maxterms (standard sums)

Row No.	A B C	Minterms	Maxterms
0	0 0 0	$A'B'C' = m_0$	$A + B + C = M_0$
1	0 0 1	$A'B'C = m_1$	$A + B + C' = M_1$
2	0 1 0	$A'BC' = m_2$	$A + B' + C = M_2$
3	0 1 1	$A'BC = m_3$	$A + B' + C' = M_3$
4	1 0 0	$AB'C' = m_4$	$A' + B + C = M_4$
5	1 0 1	$AB'C = m_5$	$A' + B + C' = M_5$
6	1 1 0	$ABC' = m_6$	$A' + B' + C = M_6$
7	1 1 1	$ABC = m_7$	$A' + B' + C' = M_7$

Write the Boolean function for $f(x, y, z)$ given below

x	y	z	f
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

$$f(x, y, z) = \bar{x}\bar{y}\bar{z} + \bar{x}\bar{y}z + x\bar{y}\bar{z} + x\bar{y}z + x\bar{y}\bar{z}$$

$$= m_0 + m_1 + m_4 + m_5 + m_6$$

$$= \underline{\underline{\Sigma m(0, 1, 4, 5, 6)}}$$

Boolean function can be represented as (i) sum of minterms and (ii) product of maxterms.

Sum of Minterms and product of maxterms expressions

x	y	z	f
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

Sum of minterms : Canonical form

$$\begin{aligned}
 F(x, y, z) &= x'y'z' + x'y'z + xy'z' + xy'z + xyz' \\
 &= m_0 + m_1 + m_4 + m_5 + m_6 \\
 &= \Sigma_m(0, 1, 4, 5, 6)
 \end{aligned}$$

Sum of product :

$$F(x, y, z) = x'y' + xy' + x'z'$$

SOP

$$y' + xz'$$

$$a + a = a$$

$$a = a + a + a + a$$

Product of maxterms : Canonical form

$$\begin{aligned}
 F(x, y, z) &= (x+y'+z).(x+y'+z').(x'+y'+z') \\
 &= M_2. M_3. M_7 \\
 &= \Pi_m(2, 3, 7)
 \end{aligned}$$

$$a + bc = (a + b).(a + c)$$

Product of sum :

$$F(x, y, z) = (x+y')(y'+z')$$

$$y' + xz'$$

0, 1, 4, 5

$$xyz$$

Rough

$$\begin{array}{c}
 \begin{array}{ccc}
 \overset{a}{\underbrace{(x + \bar{y}) + z}} & \overset{a}{\underbrace{(x + \bar{y} + \bar{z})}} & \underbrace{(\bar{x} + \bar{y} + \bar{z})}_b
 \end{array} \\
 \hline
 \begin{array}{cc}
 \underbrace{(a + z \cdot \bar{z})}_a & \underbrace{(b + x \cdot \bar{x})}_0
 \end{array} \\
 (x + \bar{y})(\bar{y} + \bar{z})
 \end{array}$$

Relationship between minterms and maxterms

- Sum of minterms : Canonical form

- $F(x, y, z) = x'y'z' + x'y'z + xy'z' + xy'z + xyz'$

$$= m_0 + m_1 + m_4 + m_5 + m_6$$

$$\boxed{=} = \Sigma (0, 1, 4, 5, 6) \checkmark = \Pi M(2, 3, 7) \checkmark$$

$$\underline{F'(x, y, z)} = \Sigma (2, 3, 7) \checkmark = m_2 + m_3 + m_7 = \Pi M(0, 1, 4, 5, 6) \checkmark$$

Taking complement on both sides and applying DeMorgan's theorem

$$F(x, y, z) = (m_2 + m_3 + m_7)' = m_2' . m_3' . m_7'$$

$$= (x'yz')' . (x'yz)' . (xyz)' = (x+y'+z) . (x+y'+z') . (x'+y'+z')$$

$$\boxed{=} = M_2 . M_3 . M_7 = \Pi (2, 3, 7)$$

$$m_j' = M_j$$

Express the Boolean function $F(a,b,c) = ab' + c'$ using Sum of minterms and Product of maxterms

- Two methods

1. Identify the missing term and include them in the expression using the postulates : $x+0 = x$, $x.1 = x$, $x+x'=1$, $x.x'=0$

2. Write the truth table from the given expression and then write sum of minterms and product of maxterms

$$\overline{a}b \cdot (\overline{1} + \overline{c})$$
$$\underline{\overline{a}bc} + \underline{\overline{a}b\overline{c}}$$

$F(a,b,c) = ab' + c'$ using method 1

$$\begin{aligned}
 & \overline{a}\overline{b}(c+\overline{c}) + \overline{c}(a+\overline{a})(\overline{b}+\overline{\overline{b}}) \\
 &= \overline{a}\overline{b}c + \overline{a}\overline{b}\overline{c} + \overline{a}\overline{c} + \overline{a}\overline{c} \\
 & \quad + \overline{a}\overline{c}(\overline{b}+\overline{\overline{b}}) + \overline{a}\overline{c}(\overline{b}+\overline{\overline{b}}) \\
 &= \overline{a}\overline{b}c + \overline{a}\overline{b}\overline{c} + \overline{a}\overline{b}\overline{c} + \overline{a}\overline{b}\overline{c} + \overline{a}\overline{b}\overline{c} + \overline{a}\overline{b}\overline{c} \\
 &= m_5 + m_4 + m_6 + m_2 + m_0
 \end{aligned}$$

$F(a,b,c) = ab' + c'$ using method 2


a	b	c	F	\overline{F}
0	0	0	1	0
0	0	1	0	1
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	1	0
1	1	0	1	0
1	1	1	0	1

$\rightarrow c=0$

$$\begin{aligned}
 F(a,b,c) &= \sum m(0, 2, 4, 5, 6) \\
 &= \pi M(1, 3, 7) \\
 \overline{F(a,b,c)} &= \sum m(1, 3, 7) \\
 &= \pi M(0, 2, 4, 5, 6)
 \end{aligned}$$


Design a combinational circuit that takes 3-bit input and generates an output high whenever the input is a prime number.

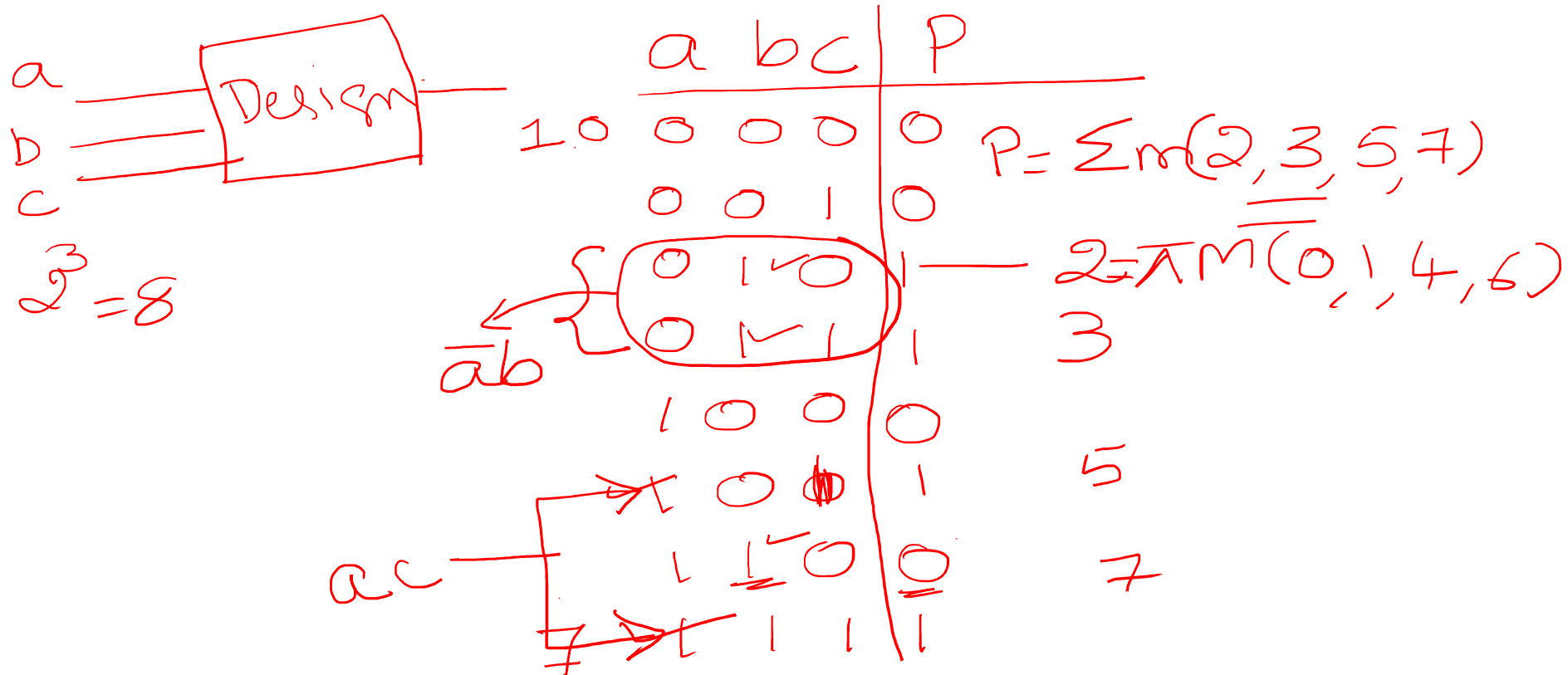Draw the circuit using basic logic gates. ✓




Rough

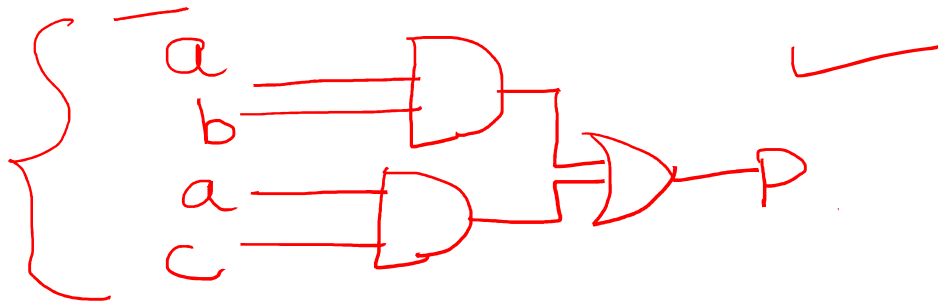
$$\begin{aligned} P(a,b,c) &= \sum m(2,3,5,7) \quad \bar{a}b \\ &= \cancel{ac} + \overbrace{\bar{a}b\bar{c} + \bar{a}bc}^{\bar{a}b} + \underbrace{\bar{a}bc + abc}_{ac} \\ &= \bar{a}b + ac \end{aligned}$$



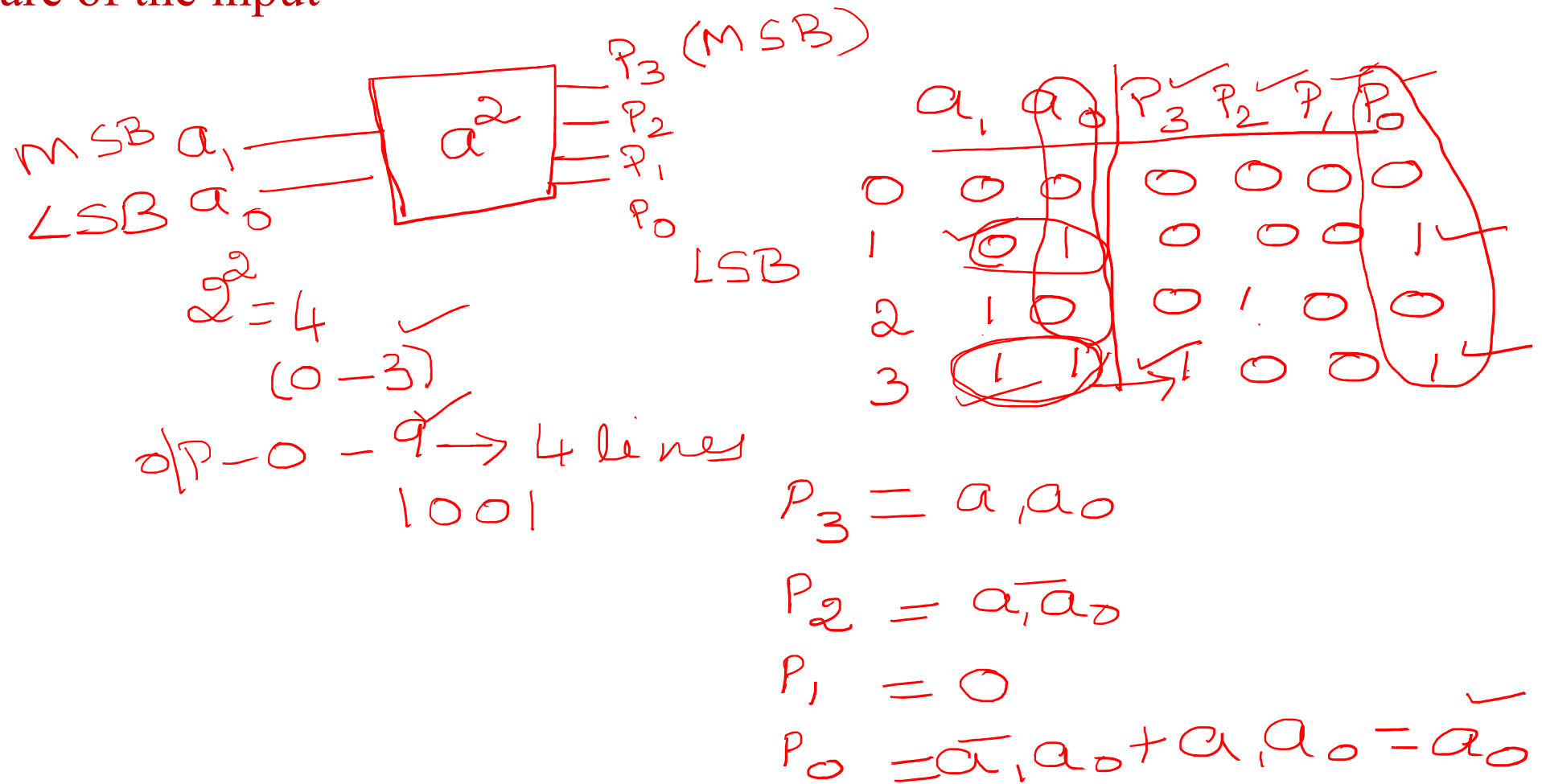Design a combinational circuit that takes 2-bit input and outputs the square of the input



Rough

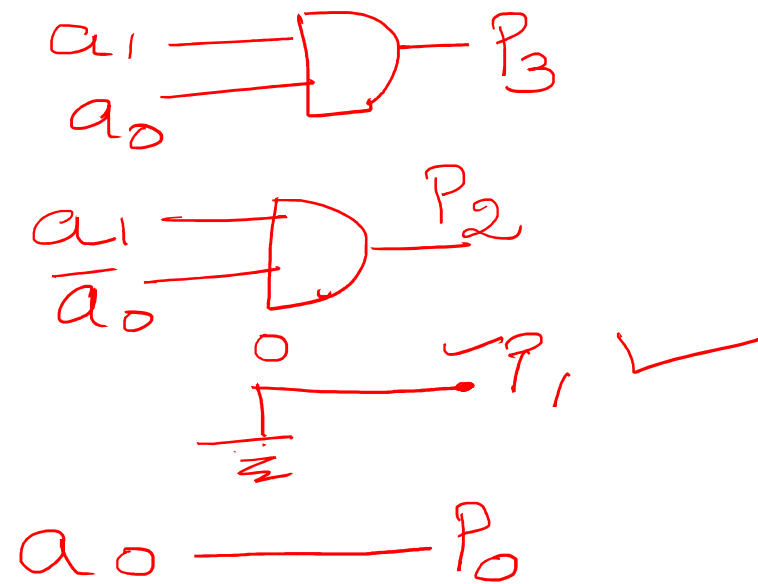

Drawing the circuit using only universal gates

- 1. $F(A,B,C,D) = \overline{AB} + \overline{CD}$ using only NAND Gates

Drawing the circuit using only universal gates

- 1. $F(A,B,C,D) = AB + CD$ using only NAND Gates

$$\underline{\underline{F}} = \overline{\overline{F}} = \overline{AB + CD} \checkmark$$


$$= \overline{\overline{AB} \cdot \overline{CD}} = \overline{X \cdot Y} \checkmark$$

Nand1 Nand2 Nand3


X Y

$$\overline{X \cdot Y} = \overline{X} \cdot \overline{Y}$$

$$F(A,B,C,D) = AB + CD$$

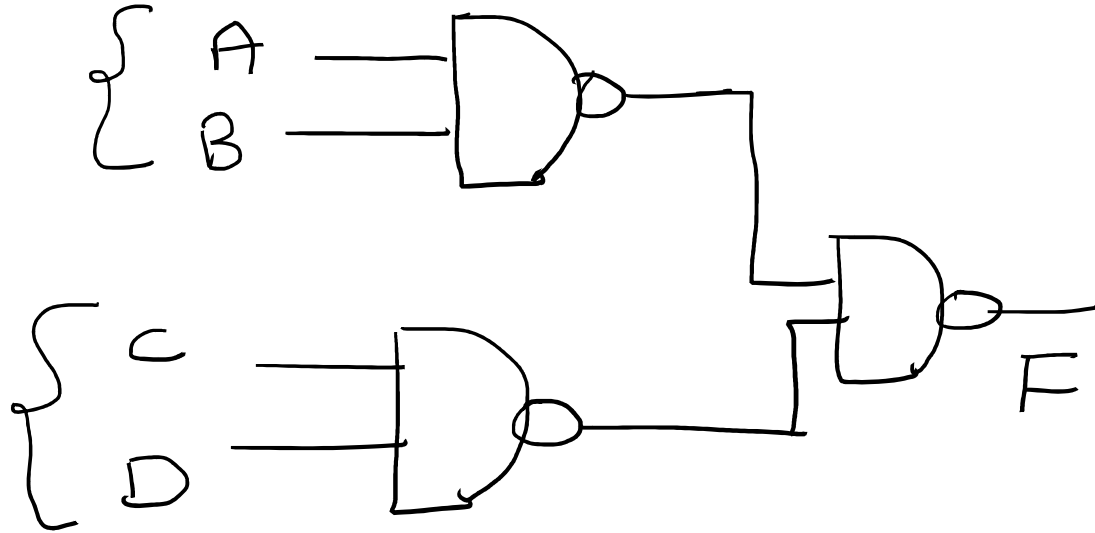


Simple way:

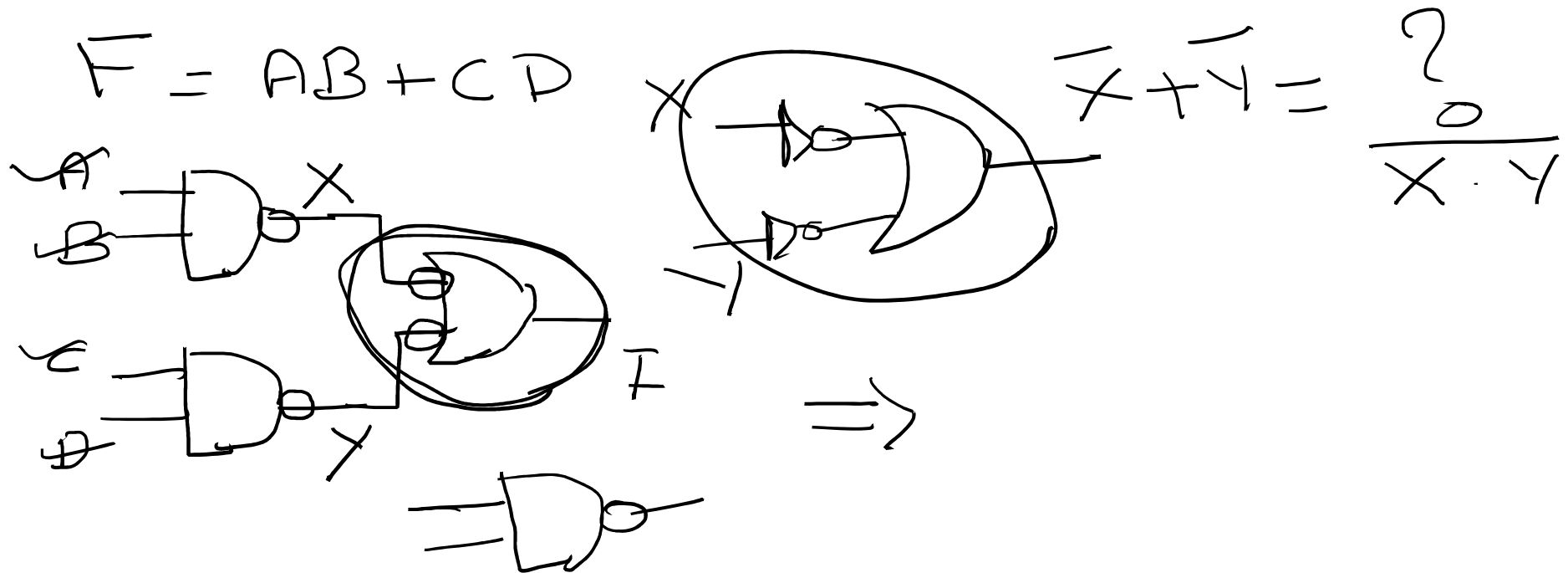

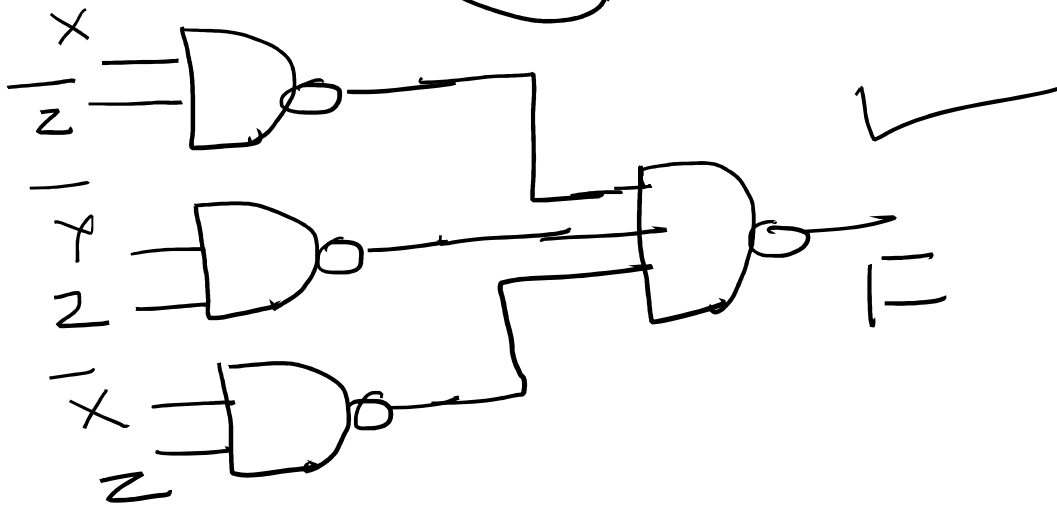2. $F(x,y,z) = xz' + y'z + x'z$ using only NAND gates

$$F(x,y,z) = \overline{x\bar{z} + \bar{y}z + \bar{x}z}$$
$$= \overline{x\bar{z}} \cdot \overline{\bar{y}z} \cdot \overline{\bar{x}z}$$




3. $F(x,y,z) = \Sigma (1,2,3,4,5,7)$ using only NAND gates

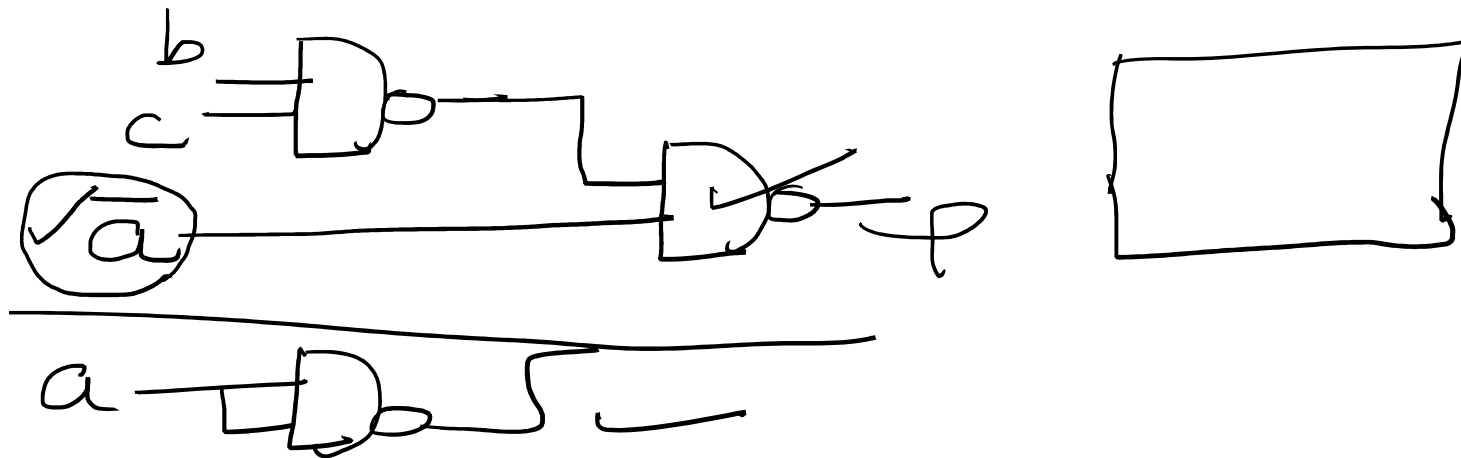4. $F(a,b,c) = a + bc$ using only NAND gates

$\overline{\overline{F}} =$

$$\overline{\overline{F}} = \overline{\overline{a + bc}} = \overline{\overline{a} \cdot \overline{bc}} \checkmark$$




Drawing the circuits using only NOR gates


- 1. $F(x,y,z) = (x+y)(y+z)$

$$\overline{\overline{F}} = \overline{(x+y) \cdot (y+z)} = \overline{\underbrace{(x+y)}_A + \underbrace{(y+z)}_B}$$


$$\rightarrow \overline{A + B}$$

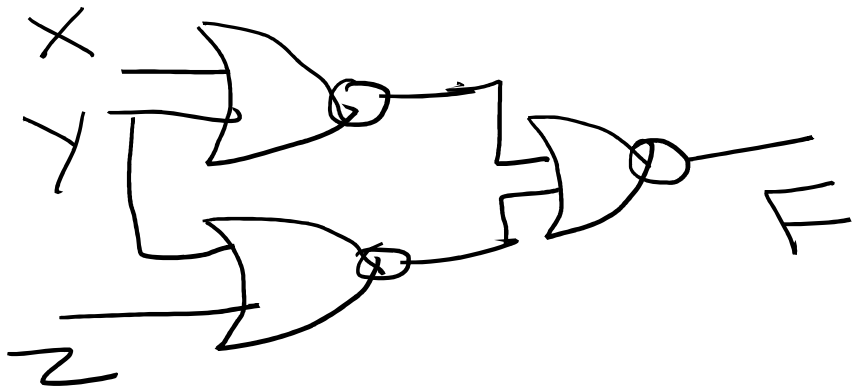

$$F = (X + Y)(Y + Z)$$

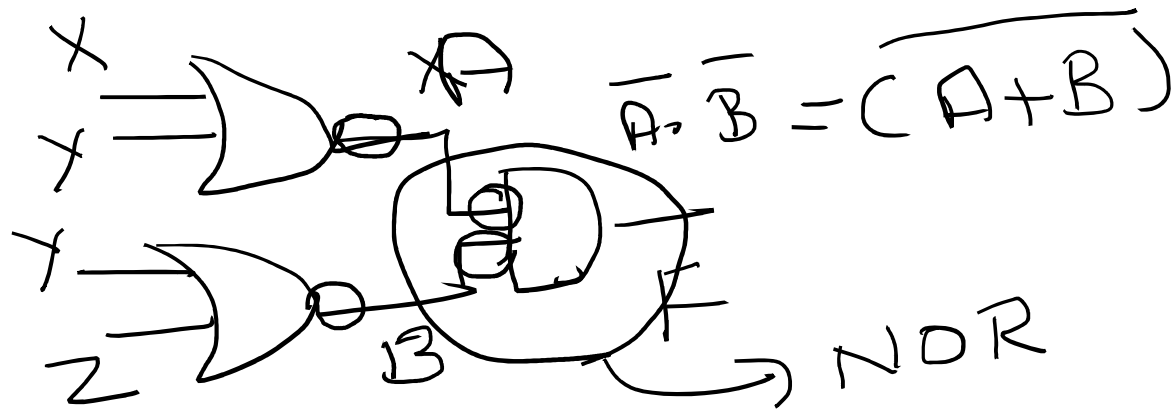

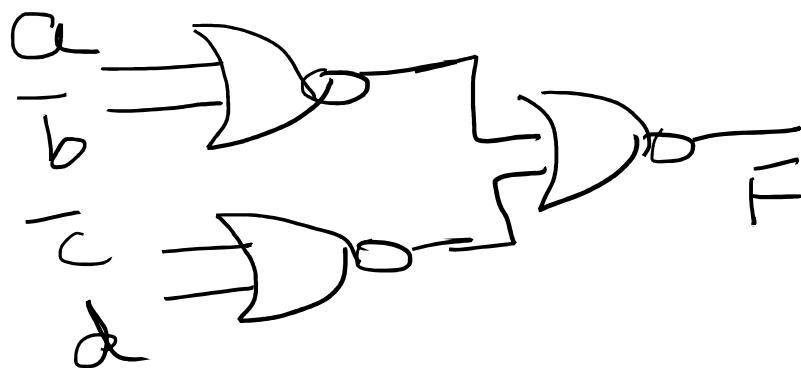
2. $F(a, b, c, d) = \underline{(a+b')}(c'+d)$




$$3. f(x,y,z) = x \cdot (y+z)$$

$$\overline{\overline{f}} = \overline{\overline{x \cdot (y+z)}}$$
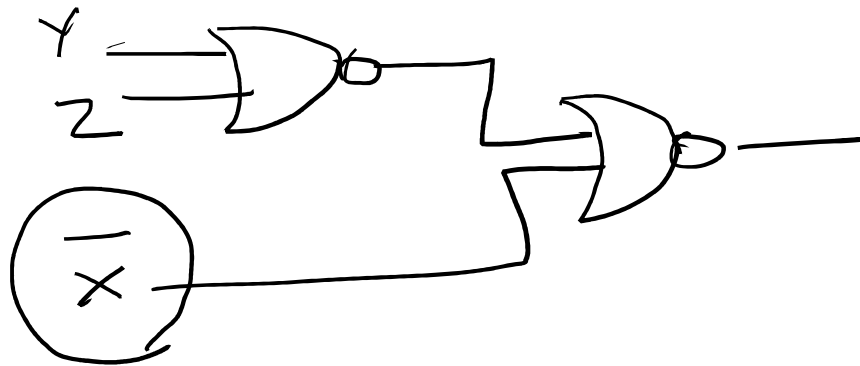
$$\overline{\overline{f}} = \overline{\overline{x \cdot (y+z)}}$$


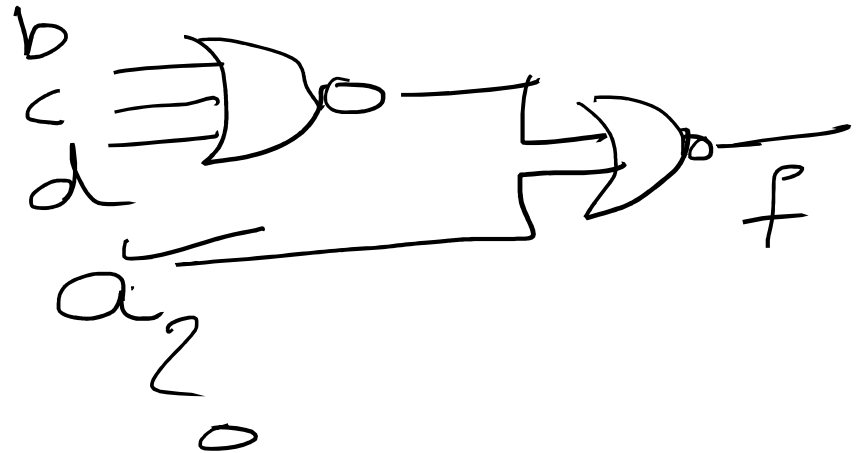
$$f(x,y,z) = \overline{a} \cdot (b+c+d)$$



4. $f(a, b, c, d) = a.b.(c+d)$

