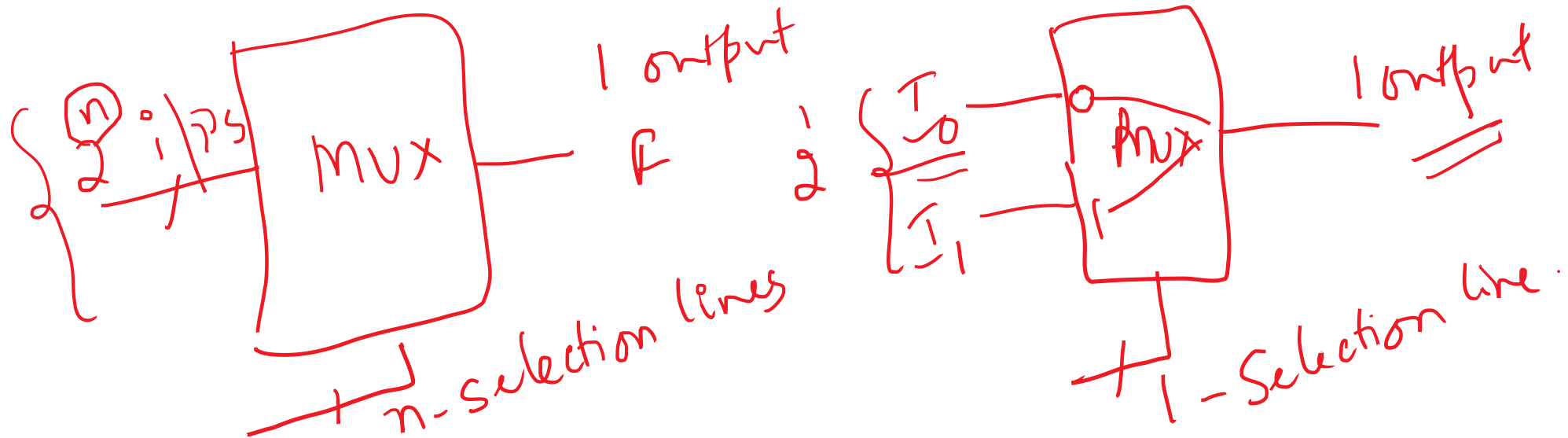


# Multiplexers


# Multiplexer

- Multiplexer is an useful MSI device and are also called as data selectors.
- Multiplexer selects one of its  $2^n$  input line and directs it to a single output line .
- n-bit select lines decide which input line is to be selected.
- Examples: 2-to-1 line MUX, 4-to-1 line MUX, 8-to-1 line MUX, 16-to-1 line MUX.



## 2-to-1 line MUX

① → select line  
2x1 MUX

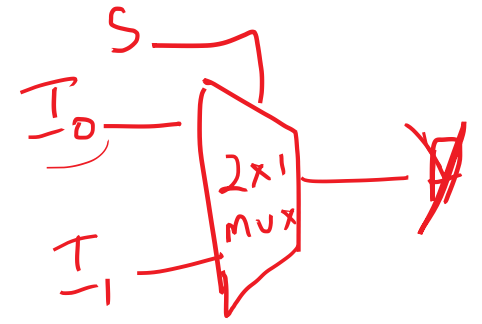

- S- selection input, y is the output, I1 and I0 are inputs
- Symbol/block diagram, function table, output expressions and circuit is given :


S	<del>Y</del>
0	I <sub>0</sub>
1	I <sub>1</sub>

$$Y = \overline{S} I_0 + S I_1$$


$$\text{When } S=0 \left\{ Y = \underline{\underline{I_0}} \right. \checkmark$$

$$\text{When } S=1 \left\{ Y = \underline{\underline{I_1}} \right.$$

# 2-to-1 line MUX

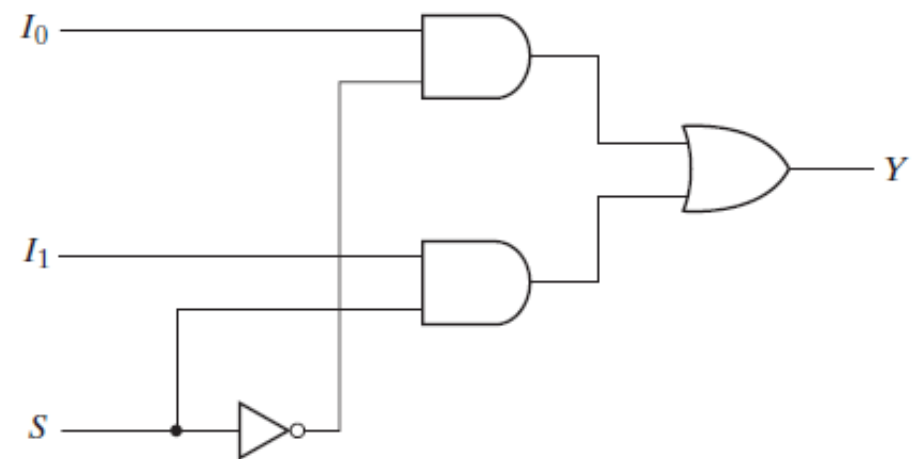

(a) Logic diagram

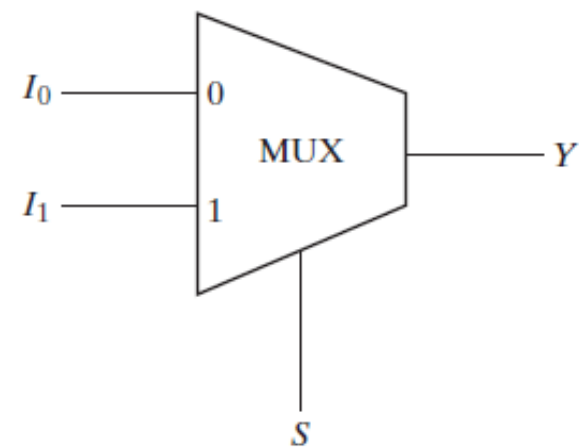


(b) Block diagram


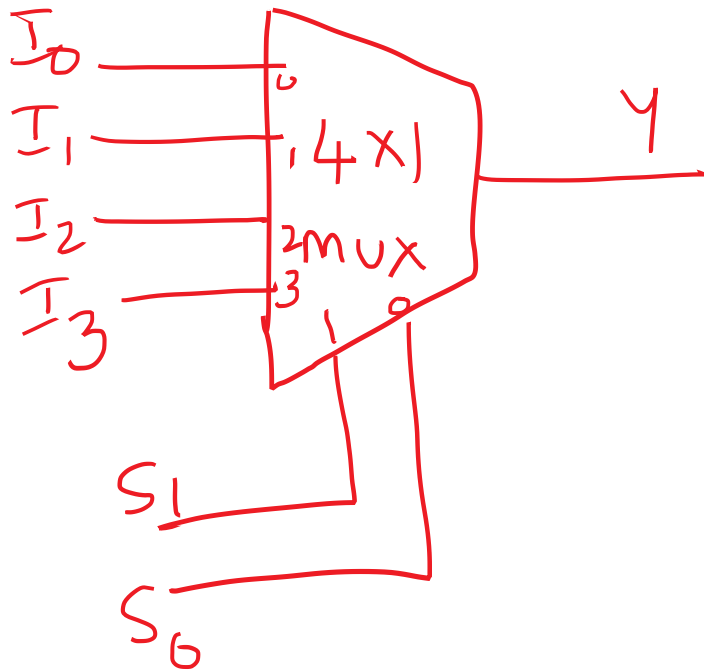
## 4-to-1 line multiplexer


- Write the Symbol/block diagram, Function table, output expressions and circuit .



$S_1$	$S_0$	$Y$
0	0	$I_0$
0	1	$I_1$
1	0	$I_2$
1	1	$I_3$


$$Y = \overline{S_1} \overline{S_0} I_0 + \overline{S_1} S_0 I_1 + S_1 \overline{S_0} I_2 + S_1 S_0 I_3$$

## 4-to-1 line multiplexer

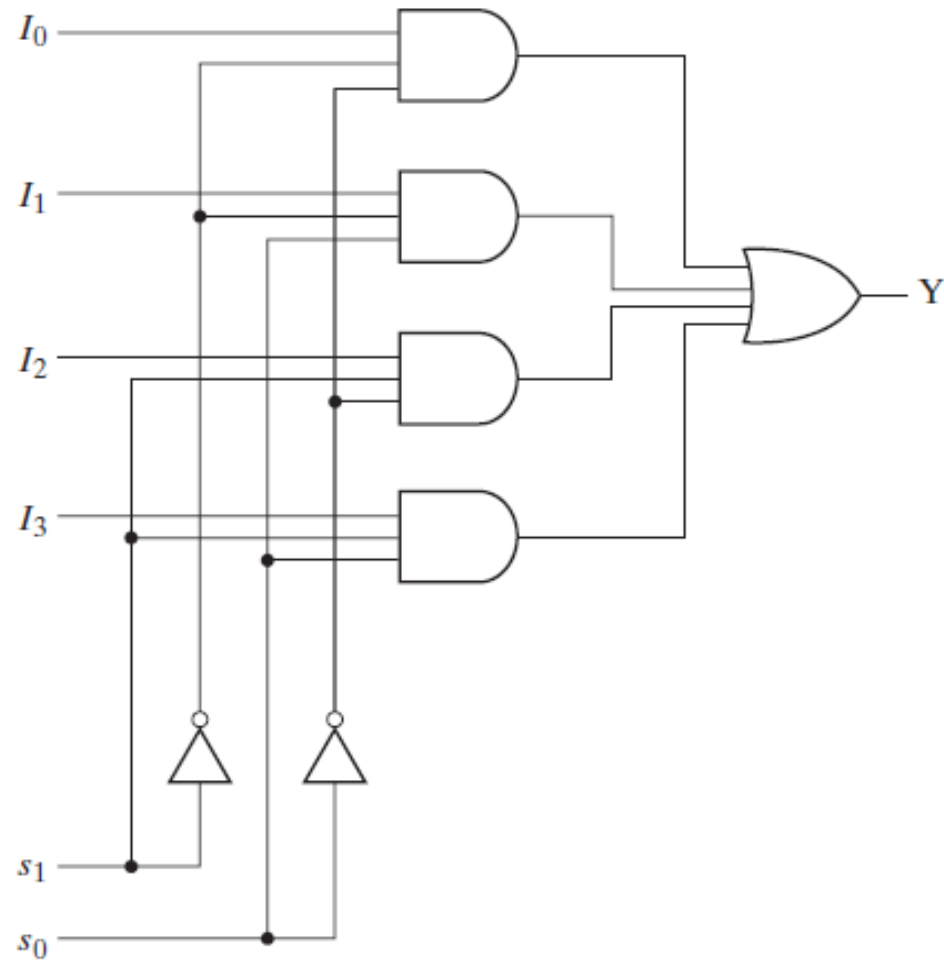
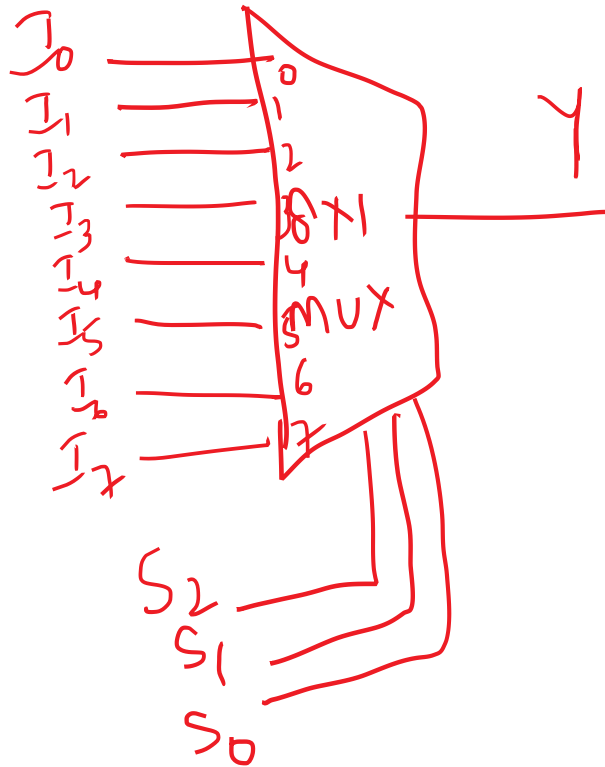
# 8-to-1 line multiplexer

- Write the Symbol/block diagram, function table, output expressions and circuit





$S_2$	$S_1$	$S_0$	$Y$
0	0	0	$I_0$
0	0	1	$I_1$
0	1	0	$I_2$
0	1	1	$I_3$
1	0	0	$I_4$
1	0	1	$I_5$
1	1	0	$I_6$
1	1	1	$I_7$

$$Y = \bar{S}_2 \bar{S}_1 \bar{S}_0 I_0 + \bar{S}_2 \bar{S}_1 S_0 I_1 + \bar{S}_2 S_1 \bar{S}_0 I_2 + \bar{S}_2 S_1 S_0 I_3 + S_2 \bar{S}_1 \bar{S}_0 I_4 + S_2 \bar{S}_1 S_0 I_5 + S_2 S_1 \bar{S}_0 I_6 + S_2 S_1 S_0 I_7$$

# Realize 4:1 using only 2:1 MUXs (Multiplexer tree)


2x1  
2x1

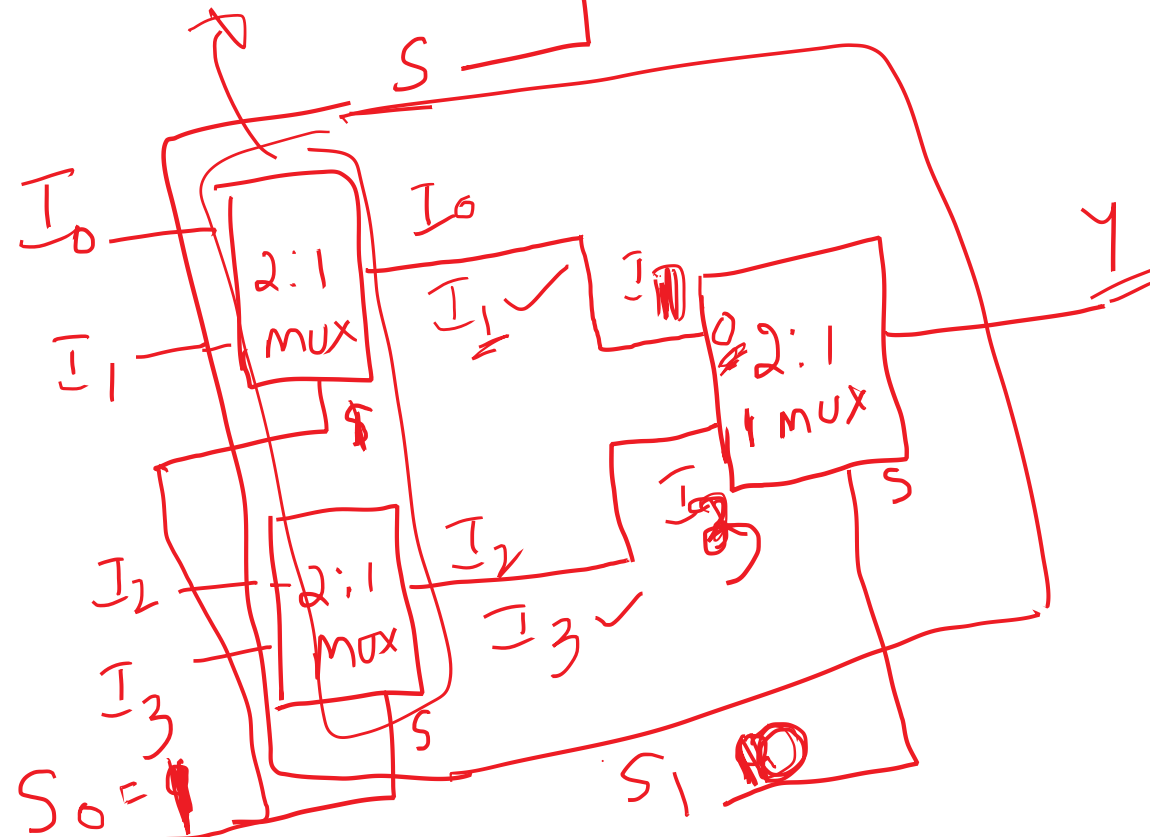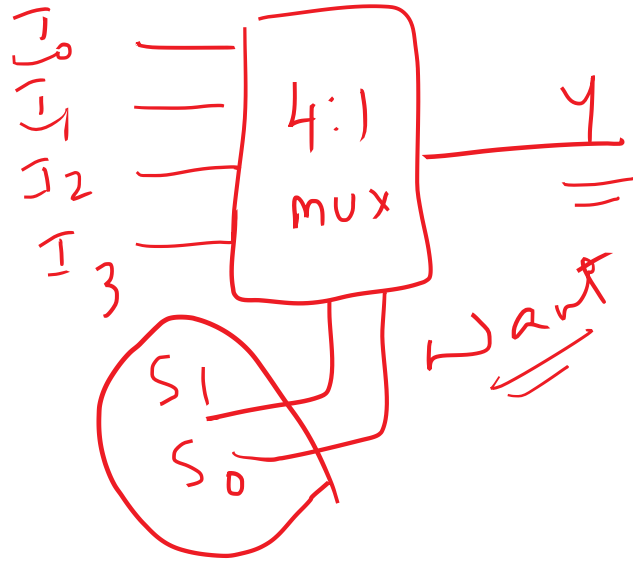


$S_1$	$S_0$	$Y$
0	0	$I_0$
0	1	$I_1$
1	0	$I_2$
1	1	$I_3$



# Realize 8:1 using only 2:1 MUXs (Multiplexer tree)

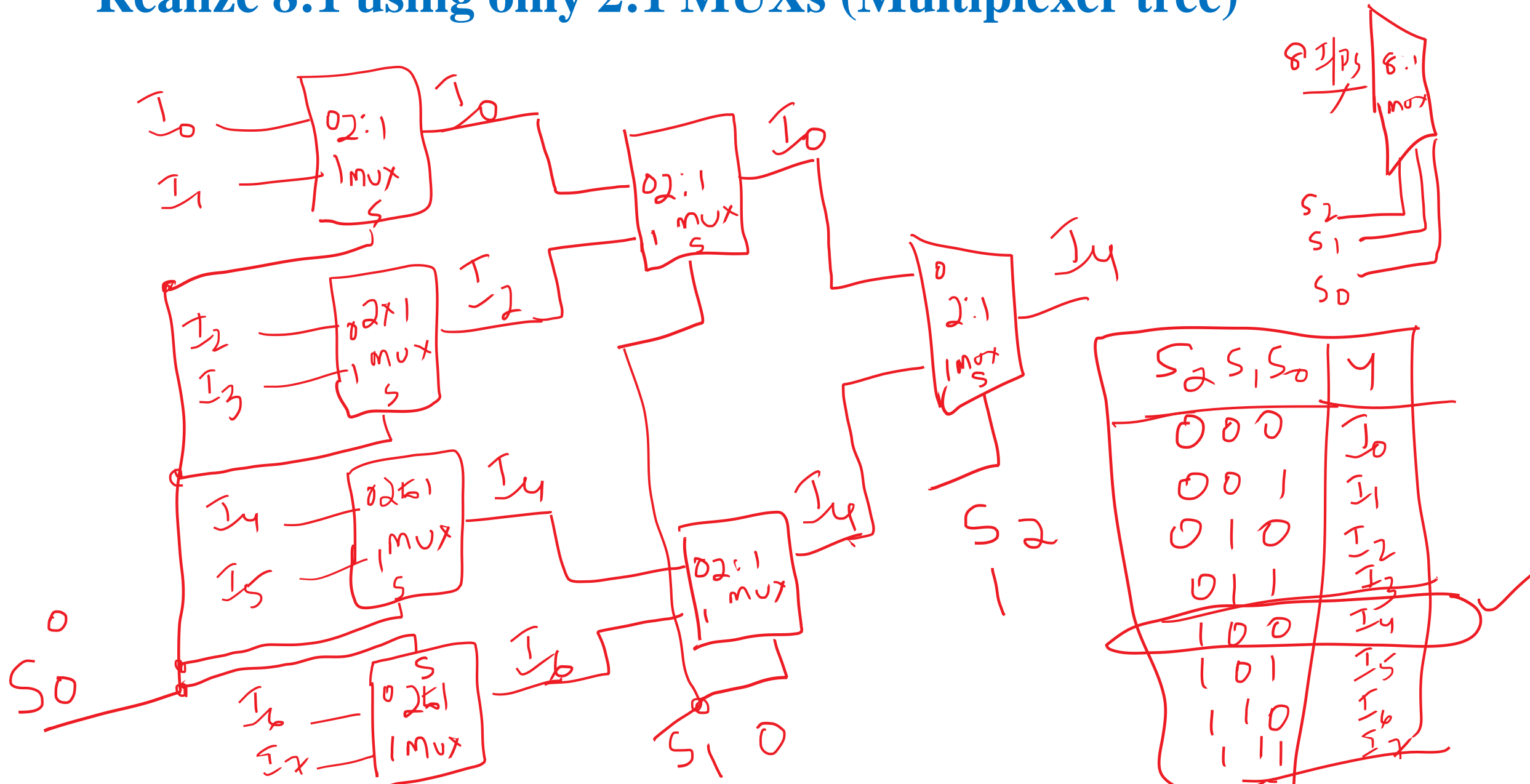


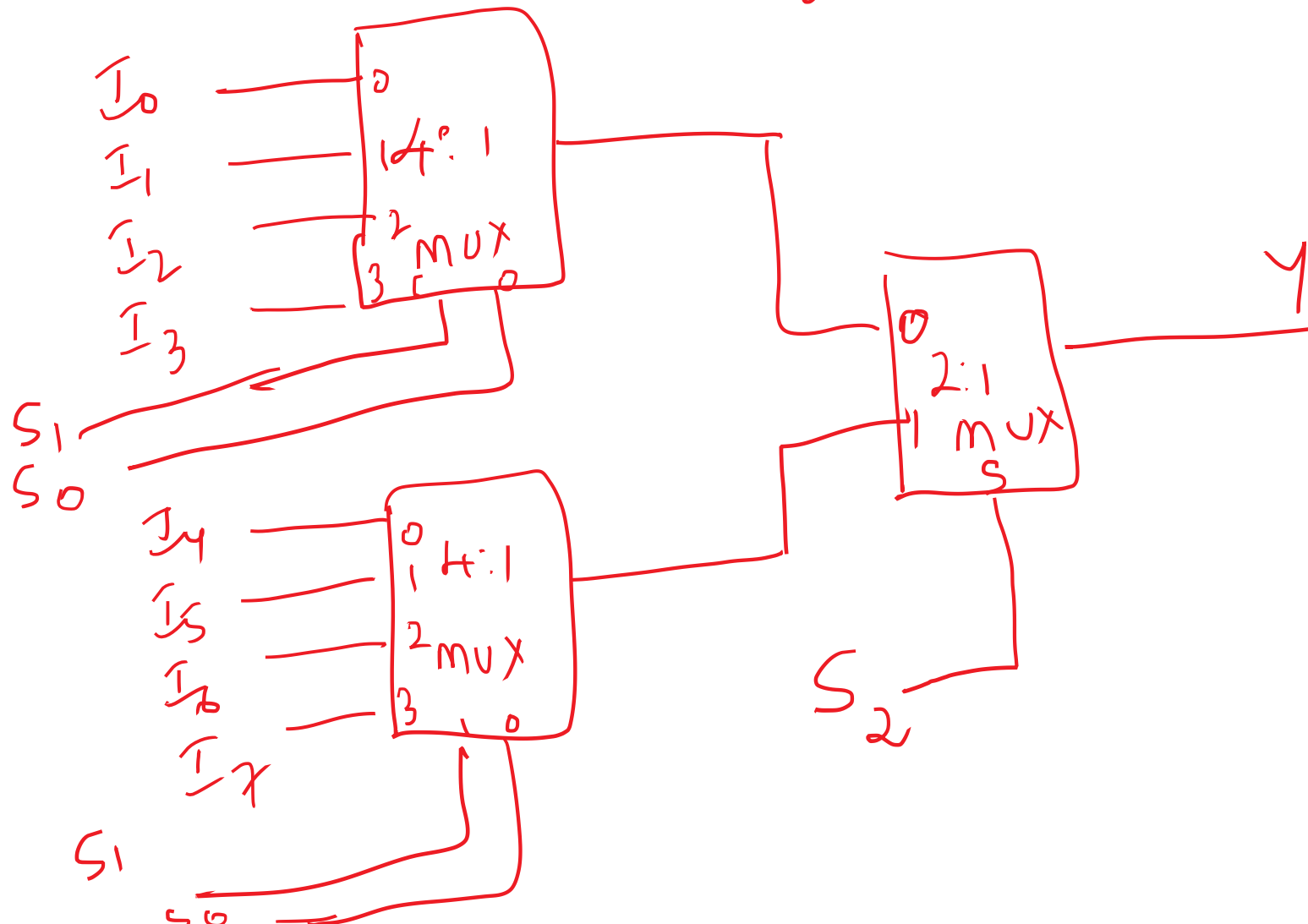Realize 8:1 using only 4:1 MUXs and 2:1 MUX


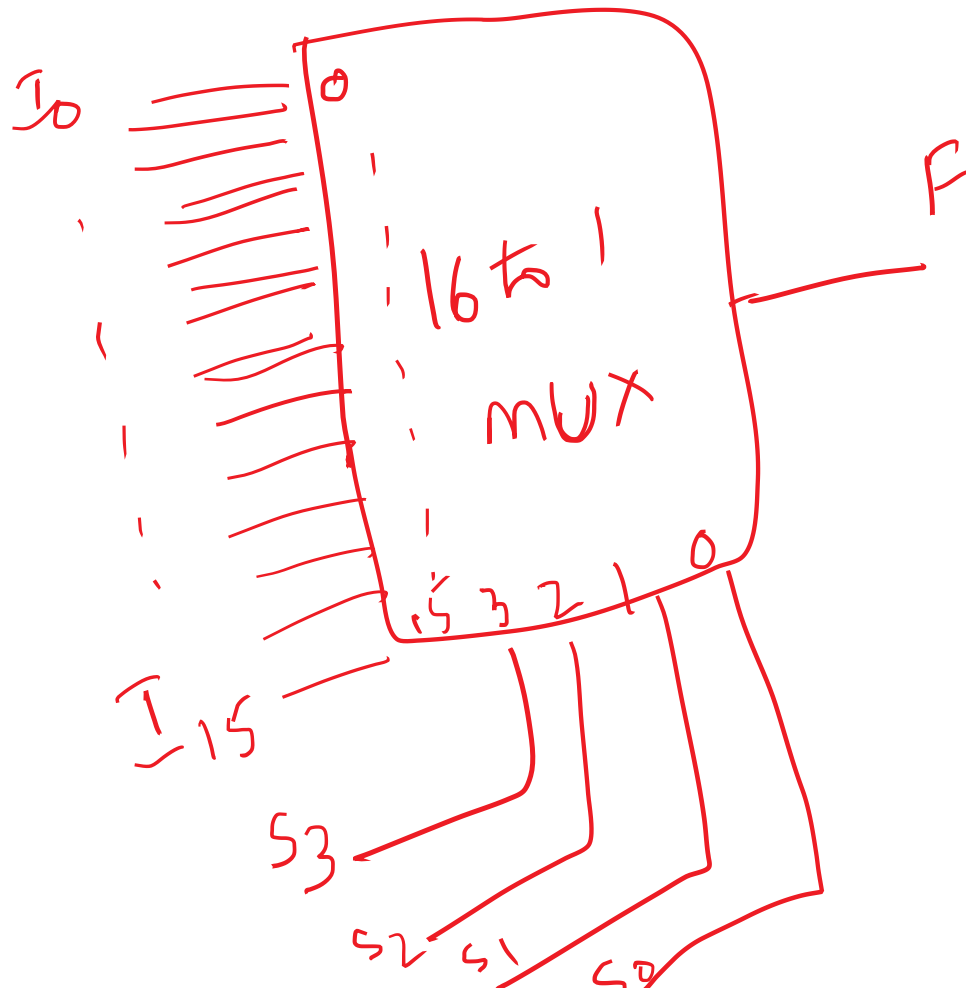
## 16-to-1 line multiplexer---Exercise for you

- Write the Symbol/block diagram, function table, output expressions and circuit



$$F = \underline{16\text{-terms}}$$

**Question?**